

Dough Creature



Dough Creature




Make a simple circuit.

Take two balls of conductive colored dough. Put insulating white clay between the balls, to prevent a short circuit. Insert a wire from the battery pack into each ball.

Find an LED bulb. Put the longer metal leg into the dough with the red wire, and the shorter leg into the dough with the black wire.

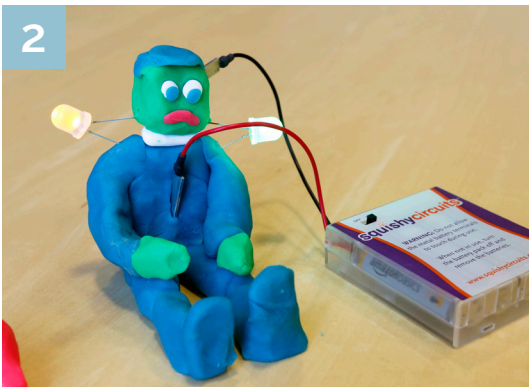
Tip: Make sure the battery pack is turned on!
Safety: Never allow the metal ends of the red and black wires to touch each other.



Build a creature that conducts electricity.

Use colored dough to make a creature, and white clay to prevent short circuits. Add a bulb, buzzer, or motor to make your creature seem alive!

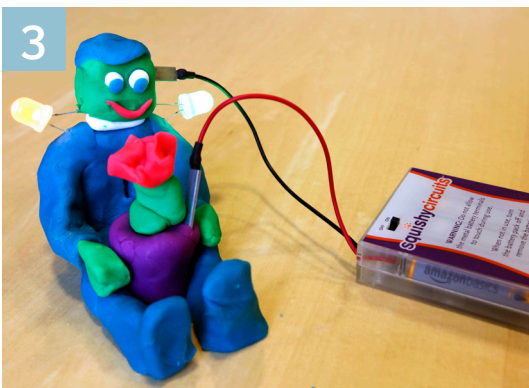*What is your creature like?
Does it get along with others?*



Tell a story.

Imagine what might happen if your dough creature lived in our world.

*What does your creature do?
Where does it live?
Who takes care of it?*